AI 시스템반도체설계 2기 RISC-V CPU

2025-08-25

JONG WAN KO (JONGWANKO@GMAIL.COM)




Contents

- Development Environment
- > RISC V Introduction
- Data Path (R, L, I, S, B, LU, AU, J, JL)
- > Type Timing (R, L, I, S, B, LU, AU, J, JL)
- Test Program : Bubble Sort
- Conclusion
- > Trouble Shooting
- ➤ Insights after finishing the project



Development Environment

- HDL : System Verilog
 - ➤ Utilized for the structural and behavioral design of the RISC-V core.
- > Software: RV32I Assembly, C
 - > Employed to implement test programs and validate the functionality of the RISC-V core.
- **EDA**: AMD Xilinx Vivado 2020.2
 - Adopted for use of RTL simulation.
- IDE: Visual Studio Code
- Supporting Tools: Online RISC-V Assembler, RVCodec.js, Compiler Explorer (Godbolt)

 



RISC - V Introduction



	Content
Designer	University of California, Berkeley
Bits	32, 64, 128
Introduced	6 August 2014 (11 years ago)
Design	RISC
Endianness	Little
Extensions	M, A, F, D, Q, etc.

Details of RISC – V Table


Simple Instruction Set

Free and Open Source

Flexible ISA Structure

 3 Important details of RISC – V Architecture





Instruction Set of RV32I

RISC-V Core Implemented in Harvard Architecture

Simple Instruction Set =>RISC Instruction

Flexible ISA Structure => **RV32I**

Free and Open Source => Anyone can design



Type	Instructions
R - Type	ADD, SUB, SLL, SRL, SRA, SLTU, XOR, AND
L - Type	LB, LH, LW, LBU, LHU
I - Type	ADDI, SLTI, XORI, ORI, ANDI, SLLI, SRLI, SRAI
S - Type	SB, SH, SW
B - Type	BEQ, BNE, BGE, BLTU, BGEU
LU - Type	LUI
AU - Type	AUIPC
J - Type	JAL
JL - Type	JALR

Control Unit

Opcode func3
regFileWe aluSrcMuxSel jalr aluControl RFWDSrcMuxSel jal branch

ROM 32 rs2 [24:20] RA2 Register File WA RD2

WA RD2

WA RD2

WData

WData

RAM wData

rData

RAM wData

rData

RAM wData

rData


rData


rData

Selected Instruction Set of RV32I

Single Cycle RISC-V Core



 

 


Single Cycle RISC-V Core

Multi Cycle RISC-V Core

	Advantage of Multi Cycle Core							
Improved Performance	Each instruction takes only as many cycles as needed. => Simple instructions finish faster than complex ones.							
Higher Clock Frequency	Since each cycle handles only a portion of the instruction, the critical path is shorter. => Faster clock design.							



 


Multi Cycle FSM

Multi Cycle RISC-V Block Diagram




R – Type Data Path

Signals	regFileWe	aluSrcMuxSel	busWe	RFWDSrcMuxSel	branch	jal	jalr
0 or 1	1	0	0	000	0	0	0

 


L – Type Data Path

Signals	regFileWe	aluSrcMuxSel	busWe	RFWDSrcMuxSel	branch	jal	jalr
0 or 1	1	1	0	001	0	0	0

 


I – Type Data Path

Signals	regFileWe	aluSrcMuxSel	busWe	RFWDSrcMuxSel	branch	jal	jalr
0 or 1	1	1	0	000	0	0	0

 

S – Type Data Path

Signals	regFileWe	aluSrcMuxSel	busWe	RFWDSrcMuxSel	branch	jal	jalr
0 or 1	0	1	1	000	0	0	0

 




➢ S –Type Data Path


B – Type Data Path

Signals	regFileWe	aluSrcMuxSel	busWe	RFWDSrcMuxSel	branch	jal	jalr
0 or 1	0	0	0	000	1	0	0

 


LU - Type Data Path

Signals	regFileWe	aluSrcMuxSel	busWe	RFWDSrcMuxSel	branch	jal	jalr
0 or 1	1	0	0	010	0	0	0

 


AU – Type Data Path

Signals	regFileWe	aluSrcMuxSel	busWe	RFWDSrcMuxSel	branch	jal	jalr
0 or 1	1	0	0	011	0	0	0

 


J – Type Data Path

Signals	regFileWe	aluSrcMuxSel	busWe	RFWDSrcMuxSel	branch	jal	jalr
0 or 1	1	0	0	100	0	1	0

 

JL – Type Data Path

Signals	regFileWe	aluSrcMuxSel	busWe	RFWDSrcMuxSel	branch	jal	jalr
0 or 1	1	0	0	100	0	1	1

 

R- Type Timing

add t1, t0, t0

```
Assembly = add x6, x5, x5

Binary = 0000 0000 0101 0010 1000 0011 0011

Hexadecimal = 0x00528333

Format = R-type
```

Operation	Expression	Decimal Result
	t0 = 5	
ADDI	t1 = t0 + t0	10

Assembly Code Test Program for I - Type



L – Type Timing

lw t2, 0(sp)

```
Assembly = sw x6, 0(x2)


Binary = 0000 0000 0110 0001 0010 0000 0011

Hexadecimal = 0x00612023

Format = S-type
```

Operation	Expression	Decimal Result
REG t2 = mem[0x30] = mem[12]		
L	t2 = 10	10

Assembly Code Test Program for L - Type

 

I – Type Timing

```
addi t0, zero, 5
```

```
Assembly = addi x5, x0, 5


Binary = 0000 0000 0101 0000 0000 0010 1001 0011

Hexadecimal = 0x00500293

Format = I-type
```

Operation	Expression	Decimal Result
	Immediate = 5	
ADDI	t0 = 5	5

Assembly Code Test Program for I - Type

 

S – Type Timing

sw t1, 0(sp)

```
Assembly = sw x6, 0(x2)


Binary = 0000 0000 0110 0001 0010 0000 0011

Hexadecimal = 0x00612023

Format = S-type
```

Operation	Expression	Decimal Result
RAM mem[sp+0] = mem[0x30] = mem[12]		
LU	RAM mem[sp+0] = $t1$	10

Assembly Code Test Program for S - Type

 

LU - Type Timing

lui t3, 0x12345

```
Assembly = lui x28, 74565


Binary = 0001 0010 0011 0100 0101 1110 0011 0111

Hexadecimal = 0x12345e37

Format = U-type
```

Assembly Code Test Program for LU - Type

Operation	Expression	Decimal Result
	Immediate = 0x12345	
LU	t3 = mem[12]	0x12345000

 



AU – Type Timing

```
auipc t4, 8

Assembly = auipc x29, 8


Binary = 0000 0000 0000 0000 1000 1110 1001 0111

Hexadecimal = 0x00008e97

Format = U-type
```

Assembly Code Test Program for AU - Type

Operation	Expression	Decimal Result
	PC = 0x0001C	
AU	t4 = PC + upper_immed	0x0000801C

 



B – Type Timing

B-type

beq t2, t1, do_jal

Assembly = beq x7, x6, 0


Binary = 0000 0000 0110 0011 1000 0000 0110 0011

Hexadecimal = 0x00638063

Operation	Expression	Decimal Result
	PC = do_jal	
AU	(t2 == t1) => PC = do_jal	0x00000028

> Test Program expected results Table

Assembly Code Test Program for B - Type

 

JAL – Type Timing

```
do_jal:
jal t5, ret_here
```

```
Assembly = jal x30, 0


Binary = 0000 0000 0000 0000 0000 1111 0110 1111

Hexadecimal = 0x00000f6f

Format = J-type
```

Assembly Code Test Program for JAL - Type

Operation	Expression	Decimal Result
	Immediate = ret_here	
JAL	t5 = PC+ 4, PC += ret_here	ret_here

 


JALR - Type Timing

Operation	Expression	Decimal Result
	JALR 0x34 => 0x3C	
JALR	PC += t4 => PC = t5 = 0x2C	0x000002C

> Test Program expected results Table

 Assembly Code Test Program for JALR - Type



R – Type Test Program

```
#include <stdio.h>
int main() {
   int a = 0;
   int b = 0;
   int c = 0;
   a = 20;
   b = 5;
   c = a + b;
                                // ADD
   c = a - b;
                                 // SUB
   c = a << b;
                                 // SLL
   c = a \gg b;
                                // SRA
   c = (unsigned)a >> b;  // SRL
   c = (a < b);
                                // SLT
   c = (unsigned)a < (unsigned)b; // SLTU</pre>
   c = a \wedge b;
                    // XOR
   c = a \mid b;
              // OR
   c = a \& b;
                                // AND
   return 0;
```

Operation	Expression	Decimal Result
	* a = 20, b = 5	
ADD	a + b	25
SUB	a - b	15
SLL	a << b	640
SRA	a >> b	0
SRL	(unsigned)a >> b	0
SLT	(a < b)	0
SLTU	(unsigned)a < (unsigned)b	0
XOR	a ^ b	17
OR	a b	21
AND	a & b	4

C Code Test Program for R - Type





L – Type Test Program

```
main:
   addi sp, x0, 16
   addi sp, sp, -16
         t1, 0xA1B2C
                              # x6 = 0xA1B2C000
   lui
   addi t1, t1, 0x000003D4
                              \# x6 = 0xA1B2C3D4
         t1, 0(sp)
                              # mem[0]
   SW
   1b
         a0, 0(sp)
                              # a0=x10 : LB
         a1, 0(sp)
                             # a1=x11 : LH
   1h
   lw
         a2, 0(sp)
                             # a2=x12 : LW
         a3, 0(sp)
                              # a3=x13 : LBU
   1bu
                              # a4=x14 : LHU
   1hu
         a4, 0(sp)
halt:
         zero, halt
   jal
```

Operation	Expression	Decimal Result
*	x6 = 0xA1B2C3D4, RAM=> me	em[0]
LB	mem[10] = 0xFFFFFFD4	0xFFFFFD4
LH	mem[11] = 0xFFFFC3D4	0xFFFFC3D4
LW	mem[12] = 0xA1B2C3D4	0xA1B2C3D4
LBU	mem[13] =0x000000D4	0x00000D4
LHU	mem[14] =0x0000C3D4	0x0000C3D4

> Test Program expected results Table





🥻 대한상광회의소


I – Type Test Program

```
main:
   addi sp, zero, 16
   addi sp, sp, -16
   # t0 = 100; t1 = 100 + (-50) = 50
   addi t0, zero, 100
   addi t1, t0, -50
   # SLTI: (-1 < 0) => 1
   addi t0, zero, -1
   slti t1, t0, 0
   # t0 = 0x0FFF; SLTIU: (4095 < 1) => 0
   lui t0, 0x1
                 # 0x00001000
                    # 0x00000FFF
   addi t0, t0, -1
   sltiu t1, t0, 1
```

Operation	Expression	Decimal Result
ADDI	100 + (-50)	0x32
SLTI	-1 < 0	1
SLTIU	4095 < 1	0

> Test Program expected results Table

Assembly Code Test Program for L - Type

 

L – Type Simulation Result (Register File Mem ,Hexadecimal)



I – Type Test Program (Cont.)

```
# XOR: 0xF0F0 ^ 0x0F0F = 0xFFFF
       t0, 0xF
                        # 0x0000F000
  addi t0, t0, 0x0F0 # 0x0000F0F0
                  # 0x00001000
       t2, 0x1
  addi t2, t2, -241 # 0x00000F0F
        t1, t0, t2
                        # -> 0x0000FFFF
  # ORI/ANDI with 0x00FF
  lui
       t0, 0x1
  addi t0, t0, 0x234
                        # 0x00001234
  ori t1, t0, 0x0FF
                        # -> 0x000012FF
       t0, 0x1
  lui
  addi t0, t0, 0x234 # 0x00001234
  andi t1, t0, 0x0FF
                        # -> 0x00000034
```

Operation	Expression	Decimal Result
XOR	0xF0F0 ^ 0x0F0F	0xFFFF
ORI	0x00001234 0x00FF	0x000012FF
ANDI	0x00001234 0x00FF	0x0000034

> Test Program expected results Table





L – Type Simulation Result (Register File Mem ,Hexadecimal)




I – Type Test Program (Cont.)

```
# Shift 1 Left 31 times -> use 0x8000_0000
addi t0, zero, 1
slli t1, t0, 31
                       # -> 0x80000000
addi t0, zero, 1
slli t0, t0, 31
                       # t0 = 0x80000000
srli t1, t0, 31
                       # -> 0x00000001
addi t0, zero, 1
slli t0, t0, 31
                    # t0 = 0 \times 800000000
srai t1, t0, 31
                       # -> 0xFFFFFFF
```

Operation	Expression	Decimal Result
SLLI	1 << 31	0x80000000
SRLI	0x80000000 >> 31	0x0000001
SRAI	0x80000000 >>> 31	0xFFFFFFF

> Test Program expected results Table



 

► L – Type Simulation Result (Register File Mem ,Hexadecimal)



S – Type Test Program

```
main :
   addi sp, zero, 16
   addi sp, sp, -16
         t0, 0xA1B2C
   lui
   addi t1, t0, 0x3D4 #t1 = 0xA1B2C3D4
        t1, 0(sp)
                       # 0xD4
   sb
                       # 0xC3D4
   sh
        t1, 4(sp)
        t1, 8(sp)
                       # 0xA1B2C3D4
   SW
halt:
   jal
         zero, halt
```

Operation	Expression	Decimal Result
SB	t1[7:0]	0xD4
SH	t1[15:0]	0xC3D4
SW	t1[31:0]	0xA1B2C3D4

> Test Program expected results Table

Assembly Code Test Program for S - Type



➤ S – Type Simulation Result (RAM Mem ,Hexadecimal)




B – Type Test Program

```
#include <stdint.h>
int main(void) {
   volatile int
                 t0 = 0; // T1 : F0
   volatile int
                 t1 = 0; // T0 : F1
   volatile int32_t a, b;
                             // signed
   volatile uint32_t ua, ub; // unsigned
   // 1) BEQ: 5 == 5
   a = 5; b = 5;
   if (a == b) { t0 = 1; t1 = 0; } else { t0 = 0; t1 = 1; }
   // 2) BNE: 9 != 9
   a = 9; b = 9;
   if (a != b) { t0 = 1; t1 = 0; } else { t0 = 0; t1 = 1; }
   // 3) BLT (signed): -1 < 1
   a = -1; b = 1;
   if (a < b) { t0 = 1; t1 = 0; } else { t0 = 0; t1 = 1; }
   // 4) BGE (signed): 0 >= 1
   a = 0; b = 1;
   if (a >= b) { t0 = 1; t1 = 0; } else { t0 = 0; t1 = 1; }
```

Operation	Expression	Decimal Result
State True: R1 : 1 R2 : 0, State False R1 : 0, R2 : 1		
BEQ	5 == 5	R1:1R2:0
BNE	9 != 9	R1:0R2:1
BLT	-1 < 1	R1:1R2:0
BGE	0 >= 1	R1:0 R2:1

Test Program expected results Table

C Code Test Program for B - Type

 

▶ B – Type Simulation Result (RAM Mem ,Hexadecimal)



LU, AU, JAL, JALR – Type Test Program (Cont.)

```
_start:

addi sp, zero, 0x100

addi sp, sp, -16

lui t0, 0xA1B2C

addi t0, t0, 0x3D4


jal ra, _jump_test

after_jal:
```

Operation	Expression	Decimal Result
LU	t0 = 0xA1B2C	0xA1B2C
AUIPC		
J		
JL	ra = 0x14	0x14

Test Program expected results Table

 C Code Test Program for LU, AU, JAL, JALR - Type



LU, AU, JAL, JALR – Type Simulation Result (RAM Mem ,Hexadecimal)



LU, AU, JAL, JALR – Type Test Program (Cont.)

```
_auicp:
    auipc t1, 0x8
    sw t1, 0(sp)
    sw ra, 8(sp)
    j halt


_jump_test:
    sw ra, 4(sp)
    la t2, _auicp
    jalr ra, 0(t2)

halt:
    j halt
```

Operation	Expression	Decimal Result
LU	t0 = 0xA1B2C	0xA1B2C
AUIPC	t1 = pc + 0x8000	0x8014
J	ra = 0x38	0x38
JL	ra = 0x14	0x14

Test Program expected results Table

 
Assembly Test Program for LU, AU, JAL, JALR - Type





LU, AU, JAL, JALR – Type Simulation Result (RAM Mem ,Hexadecimal)





Test Program : Bubble Sort

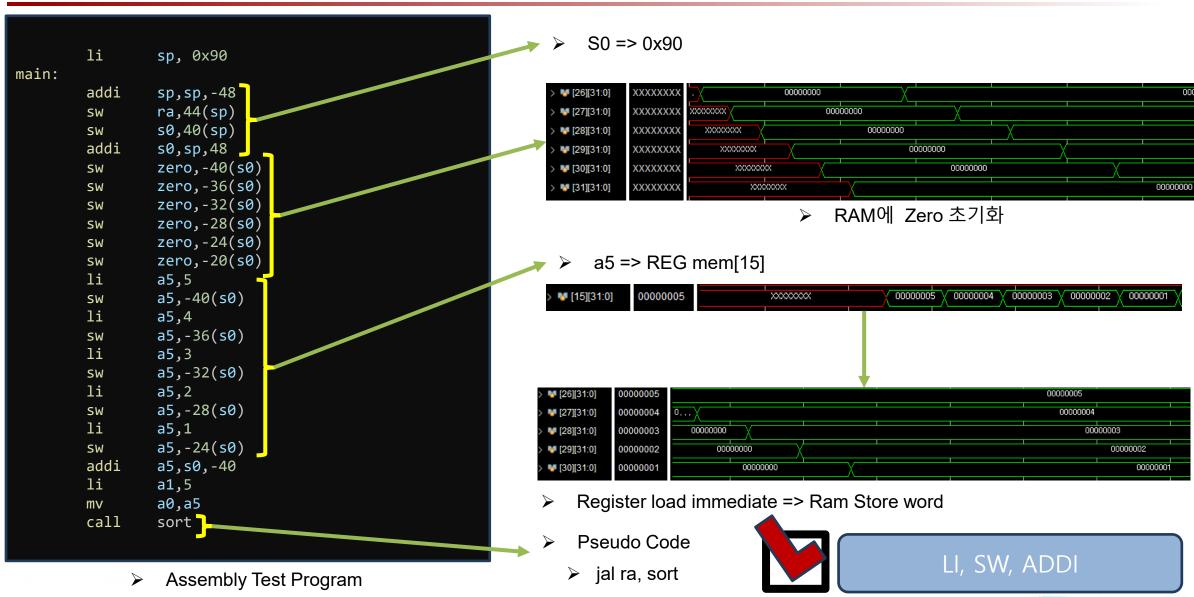

 


 

 

 

 대한상공회의소 KOREA CHAMBER OF COMMERCE AND INDUSTRY







Conclusion

Objectives and Achieved Results

Instruction Set	Objective	Implemented
R - Type	10	10
L - Type	5	5
I - Type	9	9
S - Type	3	3
B - Type	6	6
LU,AU,JAL,JL - Type	4	4

> All the assigned tasks have been successfully implemented.

Limitations and Future Development

- Pipelining
 - Future work includes introducing pipelining (2–5 stages such as IF/ID/EX/MEM/WB). This will improve instruction throughput and overall execution efficiency by overlapping stages.
- M Extension
 - > By implementing the RISC-V M extension, instructions like MUL, DIV, and REM will be supported. This adds frequently used arithmetic operations, enhancing the CPU's functionality and usability.

Trouble Shooting

Issue

- While writing assembly programs, the stack pointer (sp) often pointed to an invalid or overlapping region.
- When adding new instruction types, it was difficult to determine how to modify the datapath.

Cause

- > The RAM size was not fully considered, and the sp value was assigned arbitrarily without checking memory boundaries.
- It was unclear where to insert MUXes and which data paths should be used.

> Fix

- Investigated the available RAM size first, then calculated an appropriate initial sp value within valid memory space.
- Adjusted the datapath by carefully deciding MUX positions and data routes, ensuring both data flow correctness and control timing.

Lesson Learned

- Always check RAM capacity before assigning sp, and reserve safe stack space to prevent memory corruption.
- Careful consideration of data flow and control timing is essential when extending the datapath with new instructions.



Insights after finishing the project

From Single-Cycle to FSM

➤ At first, I could not fully understand how instructions execute in a single-cycle CPU. After restructuring the design into FSM stages (Fetch, Decode, Execute, Memory, Writeback), I gained clarity. Writing test programs and verifying each instruction step by step helped me truly grasp the CPU operation.

> Future Expectations

➤ This project will help me better understand microcontrollers (MCUs) and their internal structures. It will also make writing low-level programs, such as assembly or hardware control code, easier. I expect these skills to greatly benefit my future studies and practical projects.



Q&A